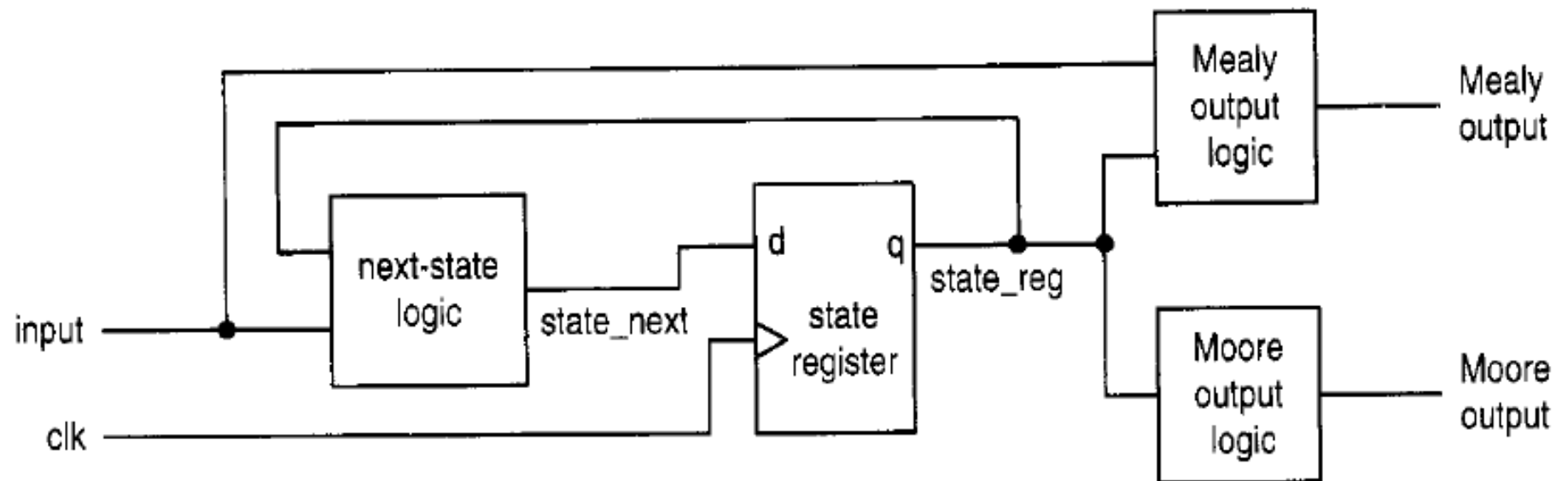


The logo consists of a light blue rounded rectangle with a thin black border. A horizontal band of medium blue color runs across the middle. The letters 'FSM' are centered in this band in a white, sans-serif font. The band is flanked by thin, light blue horizontal lines.

FSM

# Block Diagram of A Synchronous FSM




- The basic block diagram of an FSM is the same as that of a regular sequential circuit.
- It consists of a state register, next-state logic and output logic.
- An FSM is known as a *Moore machine* if the output is only a function of state.
- And is known as a *Mealy machine* if the output is a function of state and external input.

# FSM Representation

- An FSM is usually specified by an abstract *state diagram* or *ASM chart* (algorithmic state machine chart), both capturing the FSM's input, output, states and transitions in a graphical representation.
- The two representations provide the same information.
- The FSM representation is more compact and better for simple applications.
- The ASM chart representation is somewhat like a flow chart and is more descriptive for applications with complex transition conditions and actions.

# State Diagram

mo: Moore output  
me: Mealy output

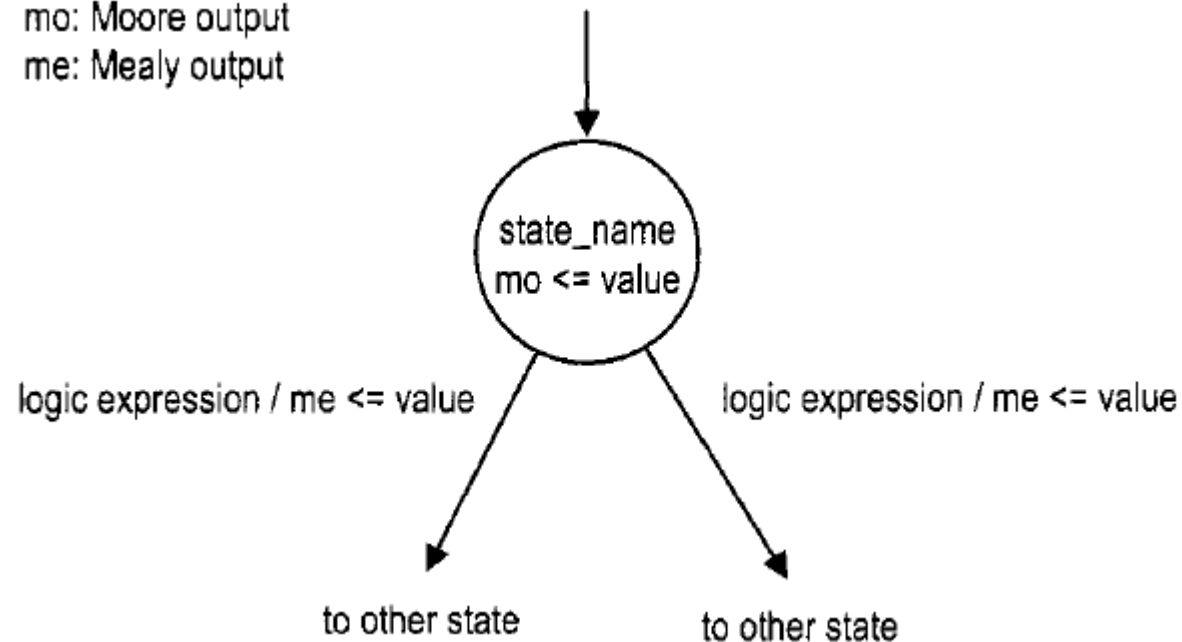


- A state diagram is composed of *nodes*, which represent states and are drawn as circles, and annotated *transitional arcs*.

- A logic expression expressed in terms of input signals is associated with each transition arc and represents a specific condition.
- The arc is taken when the corresponding expression is evaluated true.
- The Moore output values are placed inside the circle since they depend only on the current state.
- The Mealy output values are associated with the conditions of transition arcs since they depend on the current state and external input.

# FSM Code Development

- The procedure of developing code for an FSM is similar to that of a regular sequential circuit.
- We first separate the state register and then derive the code for combinational next-state logic and output logic.
- The main difference is the next-state logic.
- For an FSM, the code for the next-state logic follows the flow of a state diagram.
- For clarity and flexibility, we use the VHDL's *enumerated data type* to represent the FSM's states.

# Example of an FSM

 



- Consider the FSM of the previous slide, which has three states: s0, s1, and s2.
- We can introduced a user-defined enumerated data type as follows:

**type** eg\_state\_type **is** (s0, s1, s2);

- The data type simply lists (i.e., *enumerates*) all symbolic values.
- Once the data type is defined, it can be used for the signals, as in

**signal** state\_reg, state\_next: eg\_state\_type;

- During synthesis, software automatically maps the values in an enumerated data type to binary representations, a process known as *state assignment*.

- It consists of segments for the state register, next-state logic, Moore output logic, and Mealy output logic.

```
library ieee;
use ieee.std_logic_1164.all;
entity fsm_eg is
    port(
5      clk, reset: in std_logic;
        a, b: in std_logic;
        y0, y1: out std_logic
    );
end fsm_eg;
10
architecture mult_seg_arch of fsm_eg is
    type eg_state_type is (s0, s1, s2);
    signal state_reg, state_next: eg_state_type;
begin
15    -- state register
    process(clk, reset)
    begin
        if (reset='1') then
            state_reg <= s0;
20        elsif (clk'event and clk='1') then
            state_reg <= state_next;
        end if;
    end process;
```

```

-- next-state logic
25 process(state_reg,a,b)
begin
    case state_reg is
        when s0 =>
            if a='1' then
                if b='1' then
30                     state_next <= s2;
                else
                    state_next <= s1;
                end if;
            else
35                 state_next <= s0;
            end if;
        when s1 =>
            if (a='1') then
                state_next <= s0;
40             else
                state_next <= s1;
            end if;
        when s2 =>
45             state_next <= s0;
    end case;
end process;

```

```

-- Moore output logic
process(state_reg)
50 begin
    case state_reg is
        when s0|s2 =>
            y1 <= '0';
        when s1 =>
55         y1 <= '1';
    end case;
end process;
-- Mealy output logic
process(state_reg,a,b)
60 begin
    case state_reg is
        when s0 =>
            if (a='1') and (b='1') then
                y0 <= '1';
            else
65             y0 <= '0';
            end if;
        when s1 | s2 =>
            y0 <= '0';
70     end case;
end process;
end mult_seg_arch;

```

# FSM with merged combinational logic

An alternative code is to merge next-state logic and output logic into single combinational block.

```
architecture two_seg_arch of fsm_eg is
    type eg_state_type is (s0, s1, s2);
    signal state_reg, state_next: eg_state_type;
begin
    5    -- state register
        process(clk,reset)
        begin
            if (reset='1') then
                state_reg <= s0;
            10    elsif (clk'event and clk='1') then
                state_reg <= state_next;
            end if;
        end process;
        -- next-state/output logic
    15    process(state_reg,a,b)
        begin
            state_next <= state_reg; -- default back to same state
            y0 <= '0'; -- default 0
            y1 <= '0'; -- default 0
```


```

20      case state_reg is
        when s0 =>
            if a='1' then
                if b='1' then
                    state_next <= s2;
25                y0 <= '1';
                else
                    state_next <= s1;
                end if;
                -- no else branch
30            end if;
        when s1 =>
            y1 <= '1';
            if (a='1') then
                state_next <= s0;
35            -- no else branch
            end if;
        when s2 =>
            state_next <= s0;
        end case;
40    end process;
end two_seg_arch;

```
 
# Example: Rising Edge Detector

- The rising-edge detector is a circuit that generates a short, one-clock-cycle pulse (*tick*) when the input signal changes from '0' to '1'.
- **Moore-based design**
  - The zero and one state indicate that the input signal has been '0' and '1' for awhile.
  - The rising edge occurs when the input changes to '1' in the zero state.
  - The FSM moves to the edge state and the output, tick, is asserted in this state.





# Moore-machine based edge detector

```
use ieee.std_logic_1164.all;
entity edge_detect is
    port(
5        clk, reset: in std_logic;
        level: in std_logic;
        tick: out std_logic
    );
end edge_detect;


10 architecture moore_arch of edge_detect is
    type state_type is (zero, edge, one);
    signal state_reg, state_next: state_type;
begin
15    -- state register
    process(clk, reset)
    begin
        if (reset='1') then
            state_reg <= zero;
20        elsif (clk'event and clk='1') then
            state_reg <= state_next;
        end if;
    end process;
    -- next-state/output logic
```

```

25  process(state_reg,level)
    begin
        state_next <= state_reg;
        tick <= '0';
        case state_reg is
30             when zero=>
                    if level= '1' then
                        state_next <= edge;
                    end if;
                when edge =>
35                     tick <= '1';
                    if level= '1' then
                        state_next <= one;
                    else
                        state_next <= zero;
40                     end if;
                when one =>
                    if level= '0' then
                        state_next <= zero;
                    end if;
45             end case;
        end process;
    end moore_arch;

```

- **Mealy-based design**

 

```

architecture mealy_arch of edge_detect is
    type state_type is (zero, one);
    signal state_reg, state_next: state_type;
begin
5    -- state register
    process(clk,reset)
    begin
        if (reset='1') then
            state_reg <= zero;
10        elsif (clk'event and clk='1') then
            state_reg <= state_next;
        end if;
    end process;
    -- next-state/output logic
15    process(state_reg,level)
    begin
        state_next <= state_reg;
        tick <= '0';
    end process;
end architecture mealy_arch;

```

```

    case state_reg is
20      when zero=>
          if level= '1' then
              state_next <= one;
              tick <= '1';
          end if;
25      when one =>
          if level= '0' then
              state_next <= zero;
          end if;
    end case;
30  end process;
end mealy_arch;
```